2024 Digital IC Design Homework 1

NAME	陳育政	<u>-</u>	
Student ID	E24094198		
	Fun	ctional Simulation R	Result
Stage 1 Pass		Stage 2 Pass	Stage 3 Pass
		Stage 1	
	#		
		Stage 1 - ALU Simulation Begin	
	‡	ALU Simulation Success	
	# #	- ALU Simulation End	
		Stage 2	
	# Co # # Com #	mparater Simulation Be suparater Simulation Succession Suparater Simulation Fundamental Stage 3	egin ccess
	*	Stage 3	
	# 2-input #	Pass! // / / / / / / / / / / / / / / / / /	(/ ,0 \

Description of your design

我的作法是把 ALU 和 Q_Comparator 寫成 2 個獨立的檔案(分別為 ALU.v 及 QComp.v),又因為 HW1 是 combinational circuit,所以 2 個 module 都根據助 教提供的接線圖以 assign 方式更新 output,最後在 MAS_2input.v 檔中,呼叫 2 個 ALU module(alu_1/alu_2)以及 1 個 QComp module(q_comparator),即可達成 2-input MAS 的功能。另外,為了確保最後的 Dout 是 MSB discarded,因此 alu_2 的 Out 是暫時接到另一個 5-bit 的 tmpResult,並明確指定只有[3:0]共 4-bit 的 tmpResult 資料傳給 Dout。